
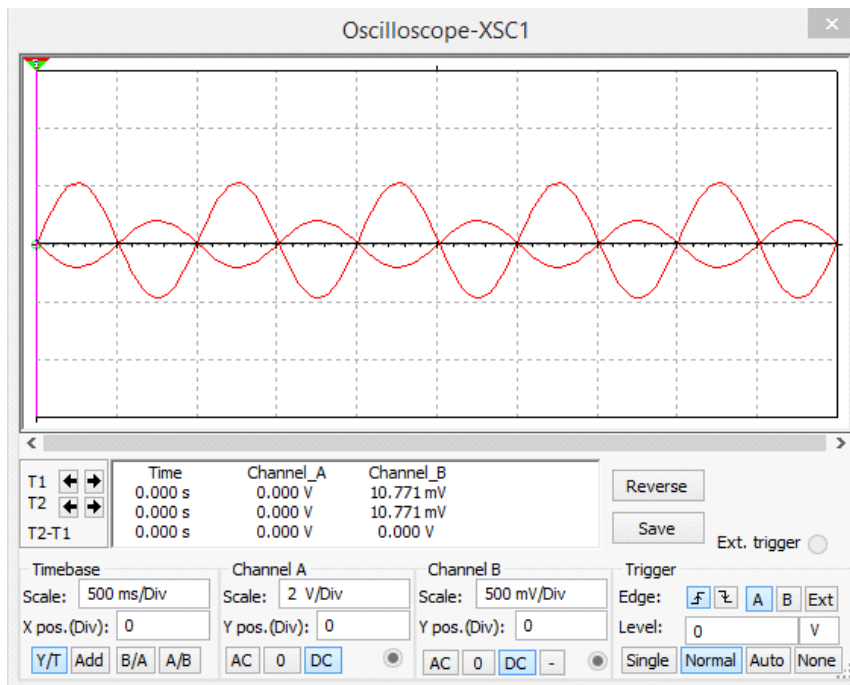


EXPERIMENT 1A: INVERTING AMPLIFIER

AIM: Study and simulation of inverting amplifier and calculate the gain using MULTISIM software worksheet

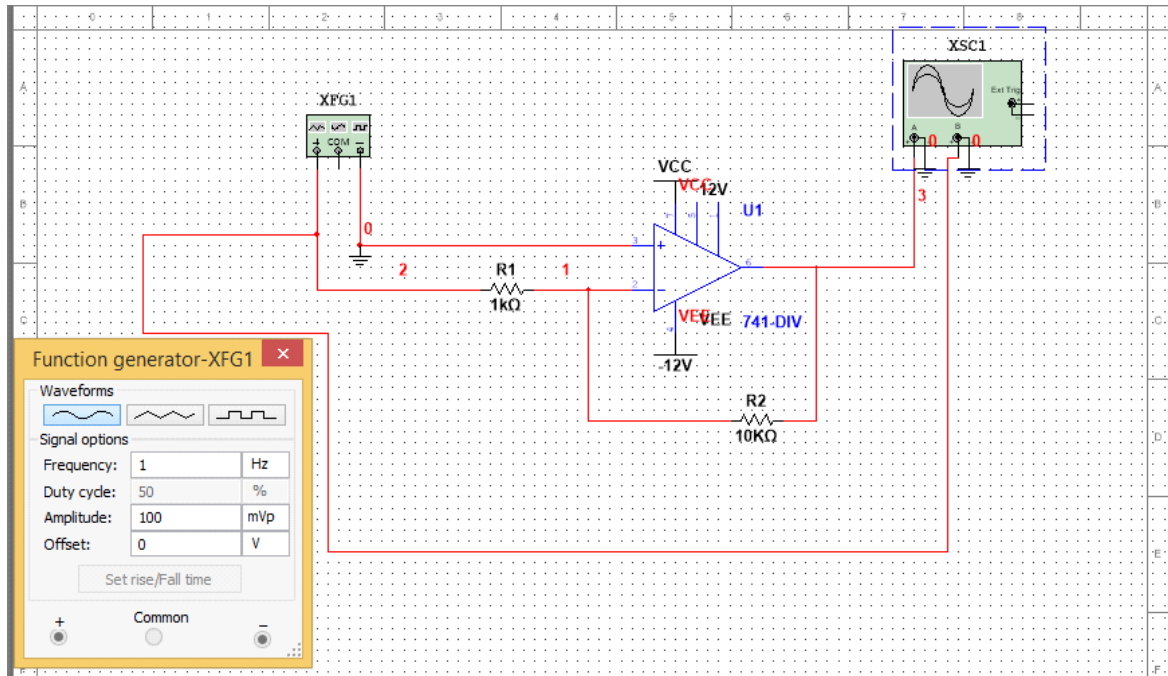COMPONENTS: 1K (R1) RESISTOR, 10 K (R2) RESISTORS, 741 IC (OP-AMP), FUNCTION GEN, OSCILLOSCOPE





$$\text{gain} = -v_o/v_{in} = -10/1 = -10$$

EXPERIMENT 1: NON INVERTING AMPLIFIER

AIM: Study and simulation of non-inverting amplifier and calculate the gain using MULTISIM software worksheet



COMPONENTS: 1K (R1) RESISTOR, 10 K (R2) RESISTORS, 741 IC (OP-AMP), FUNCTION GEN, OSCILLOSCOPE

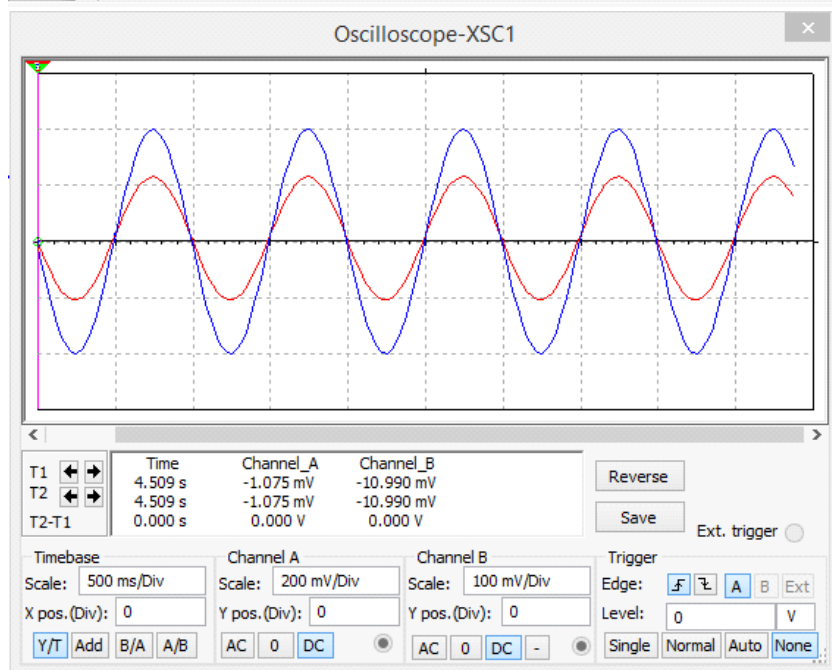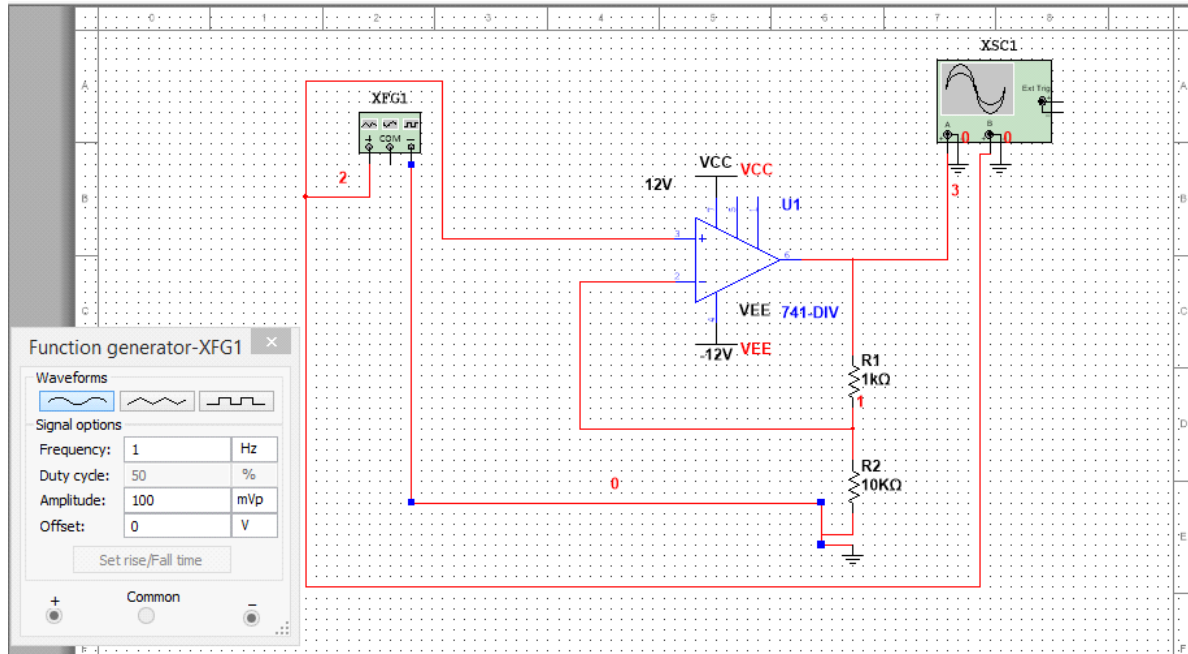

Experiment 2A: zero crossing detector

AIM: Study and simulation of zero crossing detector and observing the wave form using MULTISIM software worksheet



COMPONENTS: 1K (R1) RESISTOR, 1K (R) RESISTORS, 741 IC (OP-AMP), OSCILLOSCOPE

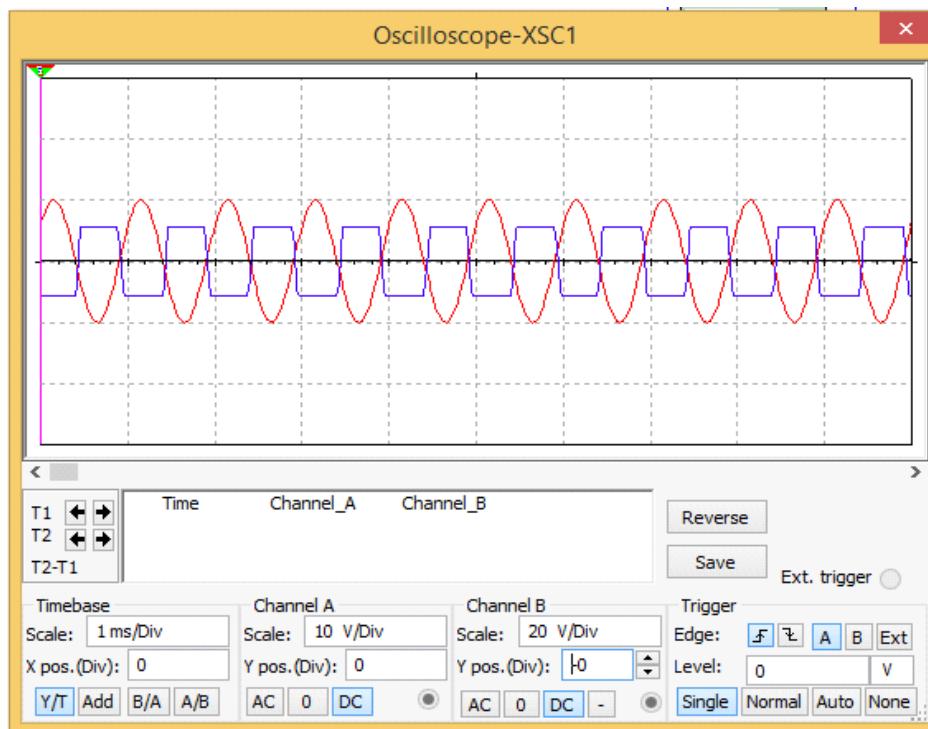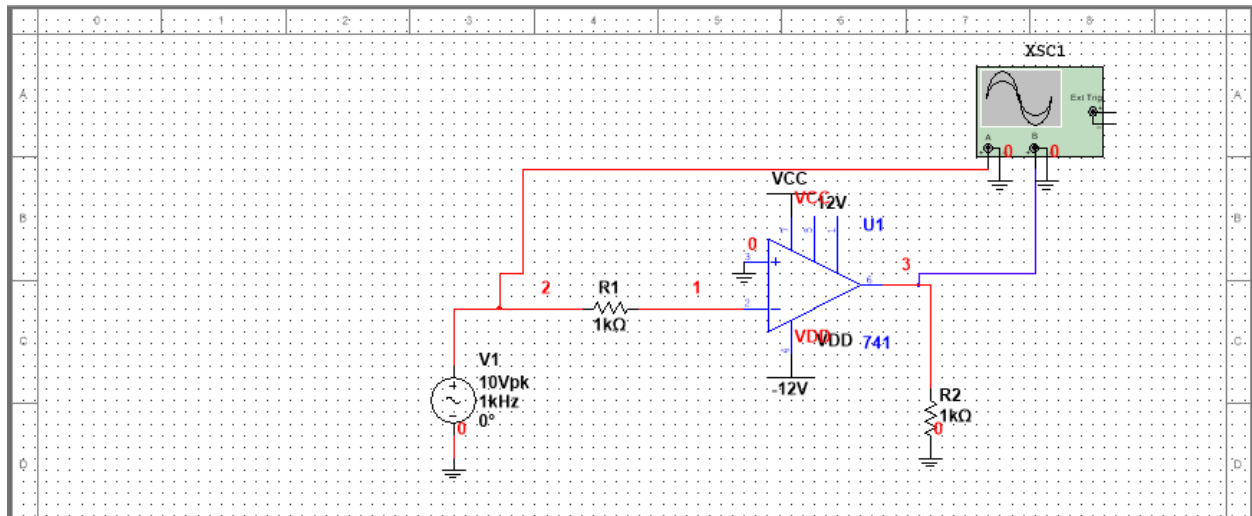

Experiment 2B: IC VOLTAGE REGULATOR

AIM: Study and simulation of IC VOLTAGE REGULATOR and observing the output voltage using MULTISIM software worksheet

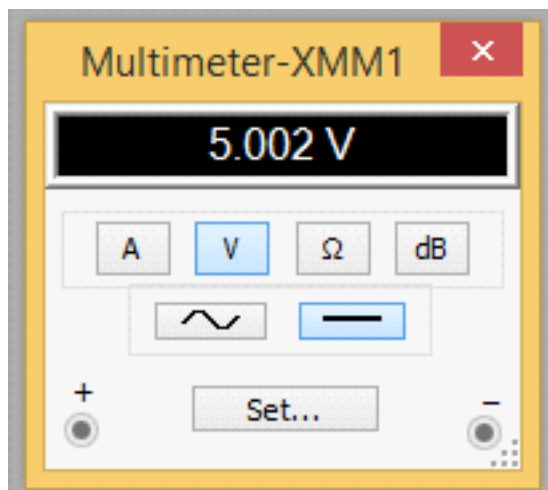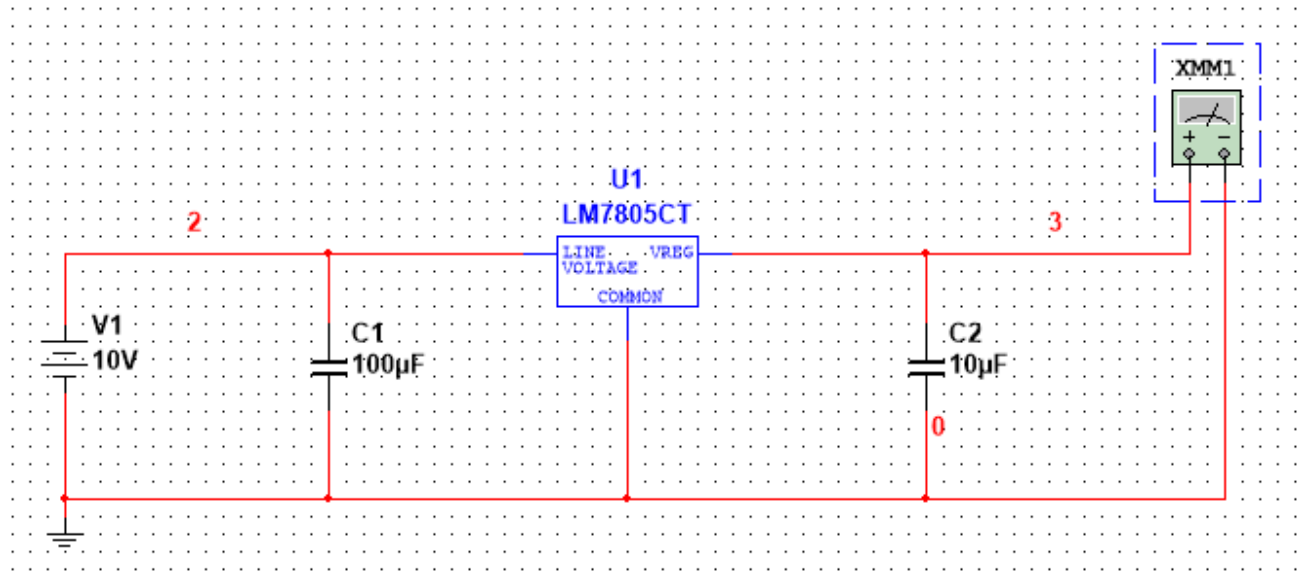COMPONENTS: DC POWER SOURCE(10V),C1(100UF),C2(10UF),MULTIMETER,LM7805CT(IC)




INPUT VOLTAGE	OUTPUT VOLTAGE
10V	5.02V
12V	5.02V
14V	5.02V
20V	5.02V

Experiment 3A: HALF WAVE PRECISION RECTIFIER

AIM: Study and simulation of HALF WAVE RECTIFIER and observing the output WAVEFORM using MULTISIM software worksheet



COMPONENTS: 2 DIODE 1N4001GP, IC 741, 10K,10K, 4.7K1KOHM(RESISTOR), CRO, FUNCTION GEN

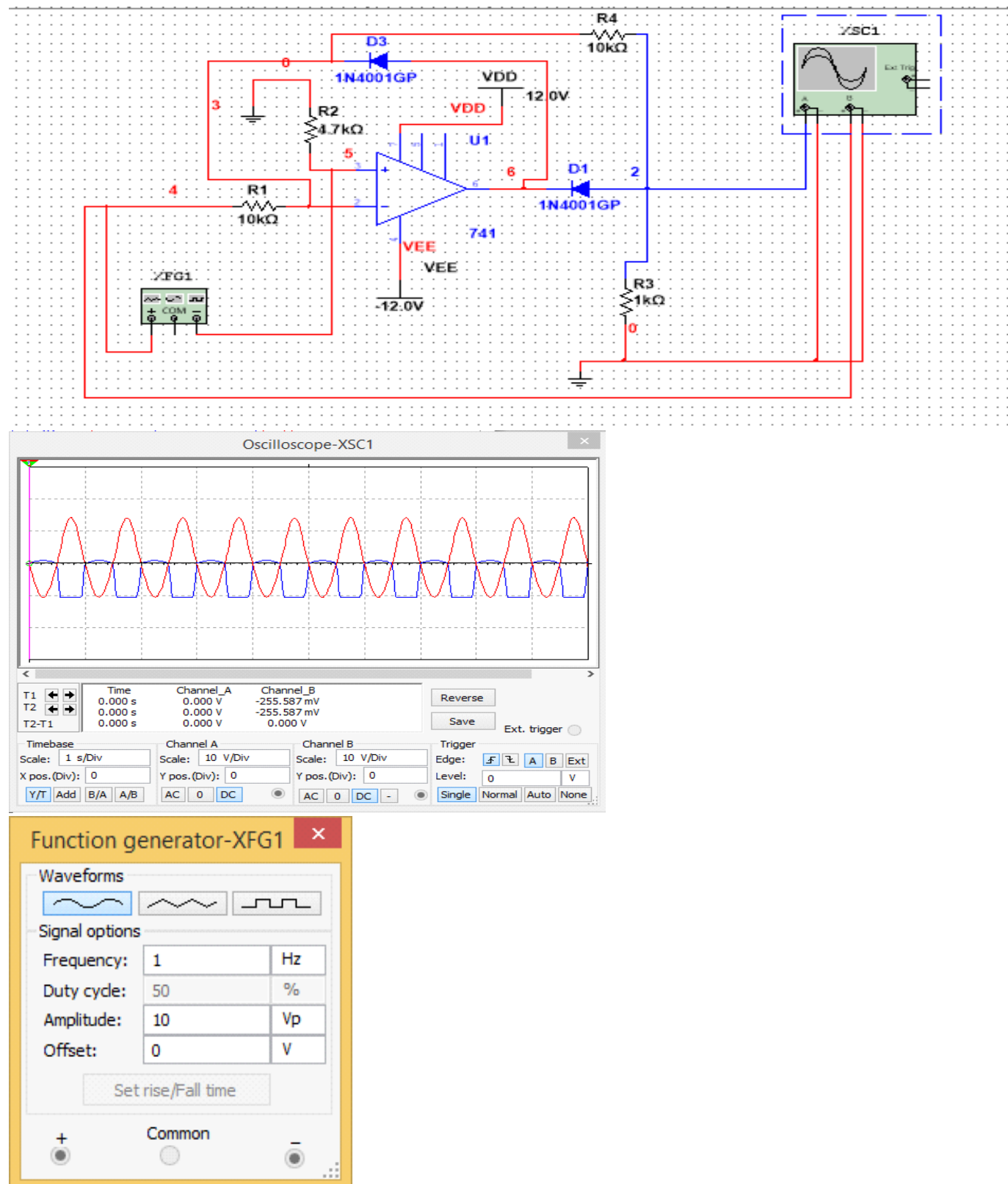

Experiment 3B: FULL WAVE PRECISION RECTIFIER

AIM: Study and simulation of FULL WAVE RECTIFIER and observing the output WAVEFORM using MULTISIM software worksheet

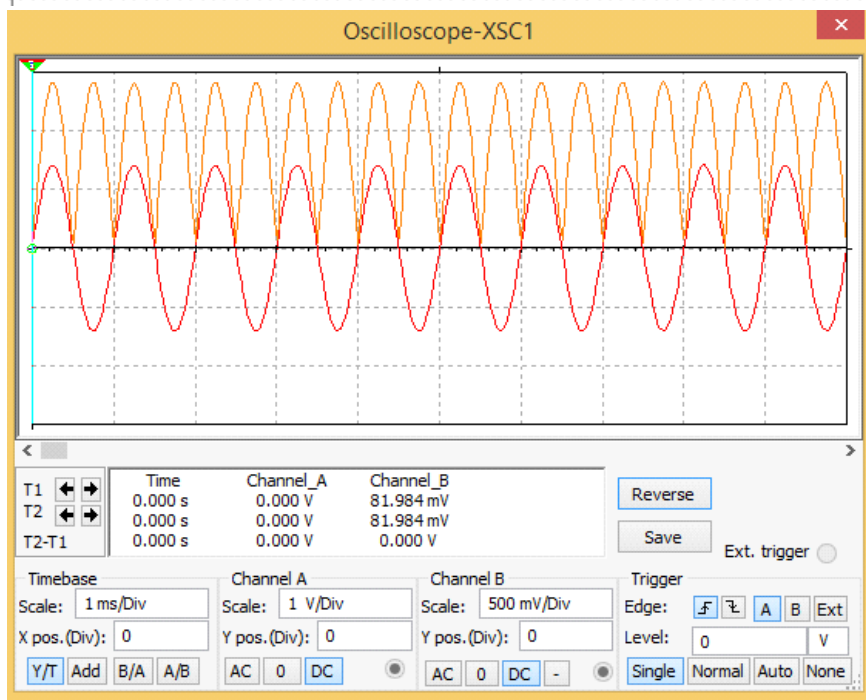
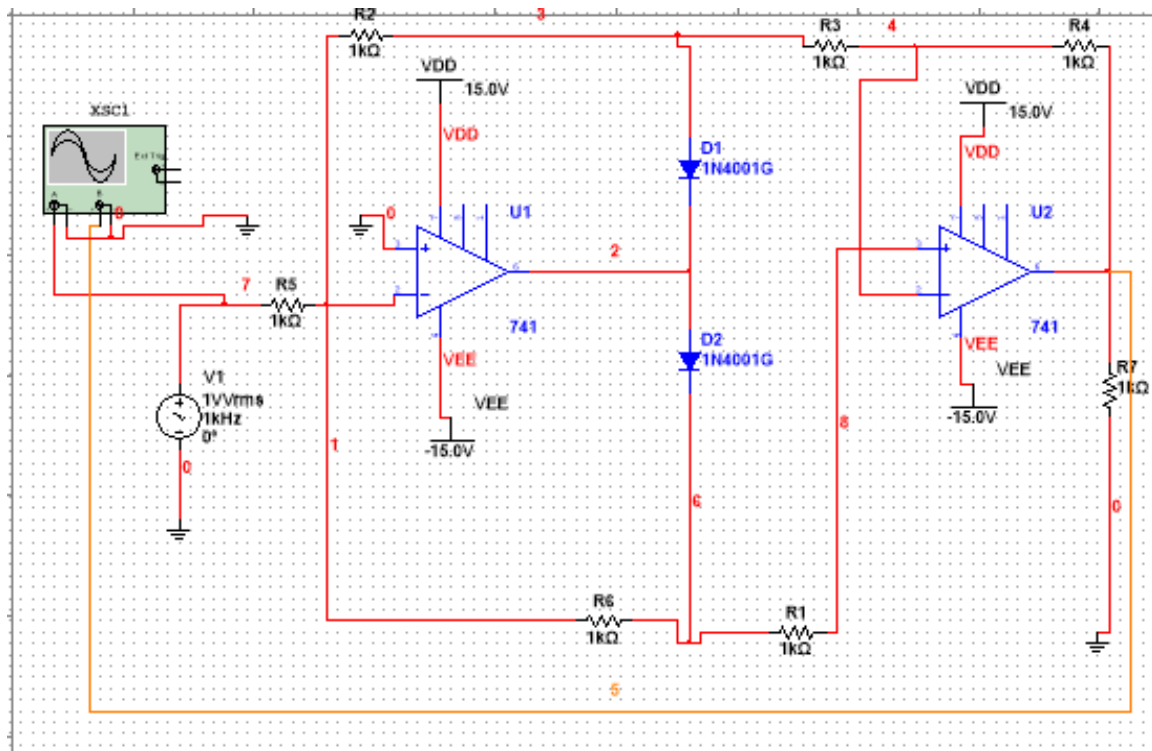
COMPONENTS: 2 (DIODE) 1N4001GP, 2 IC 741, 1K ohm(7 RESISTOR), CRO, FUNG GEN, AC power source



Experiment: 4A) FIRST ORDER ACTIVE Low Pass Filter

AIM: Study and simulation of First Order Low Pass filter and observing the output WAVEFORM using MULTISIM software worksheet

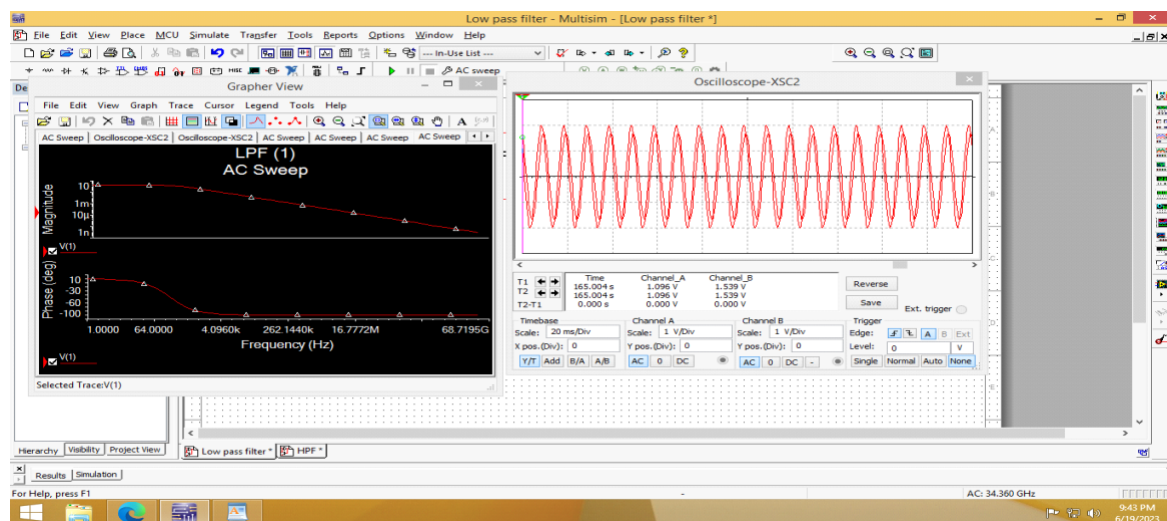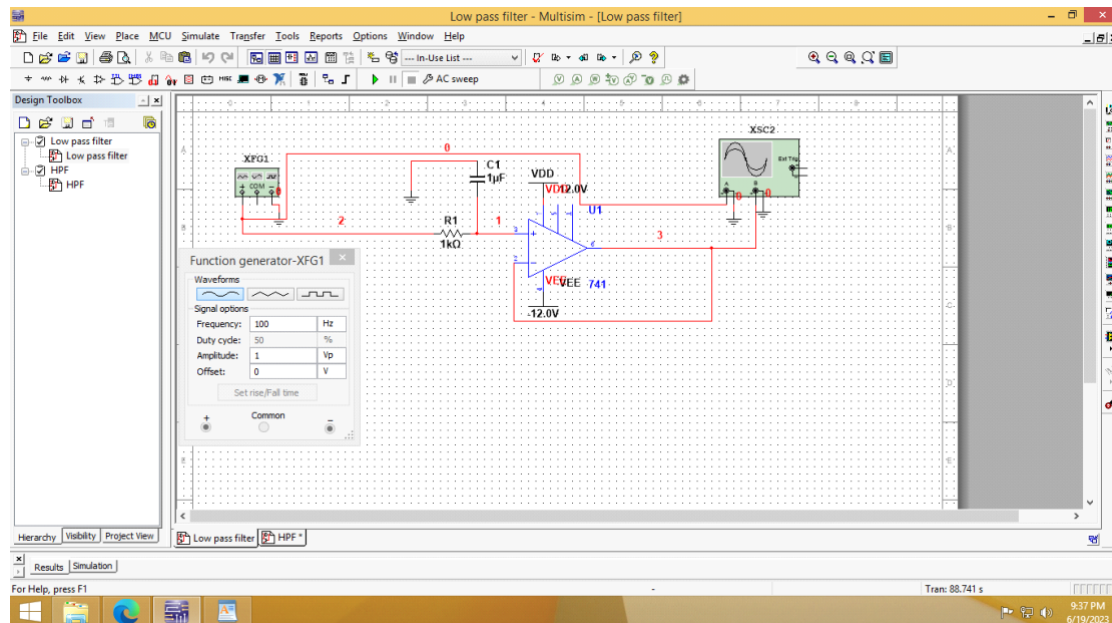COMPONENTS: 1 Micro farad (1 capacitor), IC 741, 1K ohm(1 RESISTOR), CRO, FUNC GEN



$$V_{out} \longrightarrow f_{req} \longrightarrow f_{cutoff} (f_c)$$



$$f_c = \frac{1}{2\pi R_1 C_1} = \frac{1}{2 \times 3.14 \times (1 \times 10^3) \times (1 \times 10^{-6})}$$

$$= \frac{1}{0.00628} = 159.24 \text{ Hz}$$

Experiment: 4B) FIRST ORDER ACTIVE High Pass Filter

AIM: Study and simulation of First Order High Pass filter and observing the output WAVEFORM using MULTISIM software worksheet

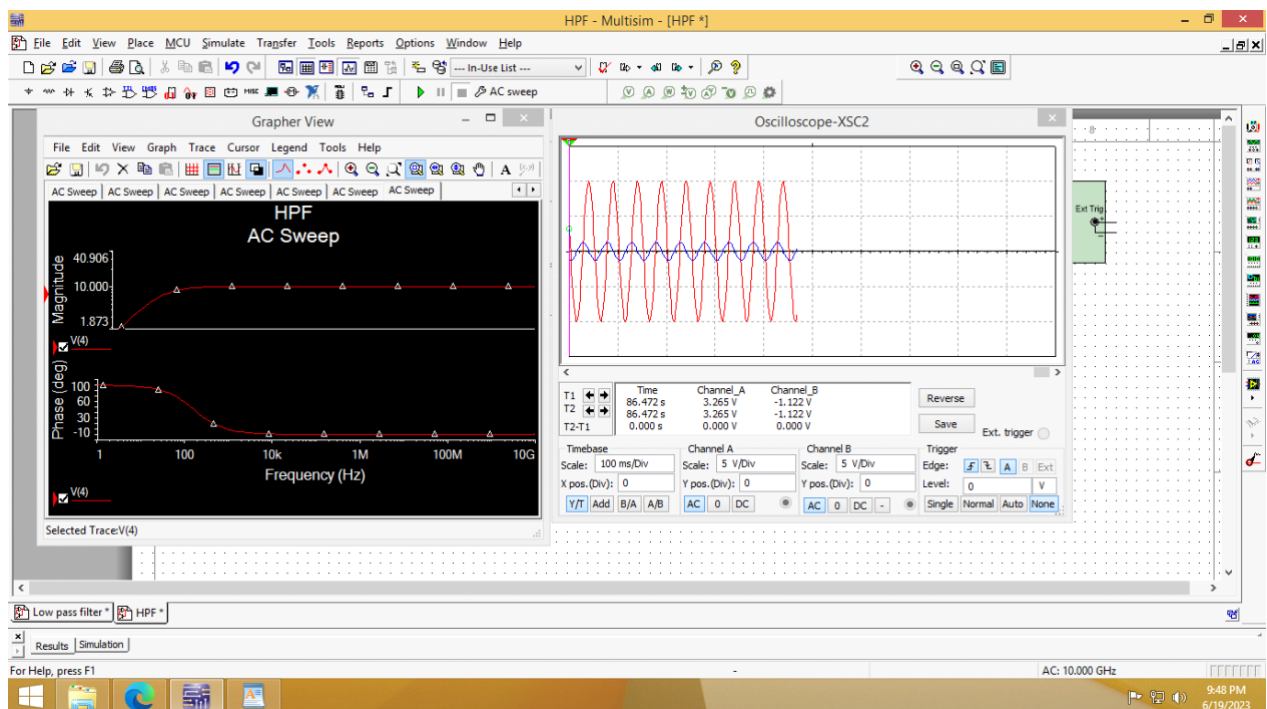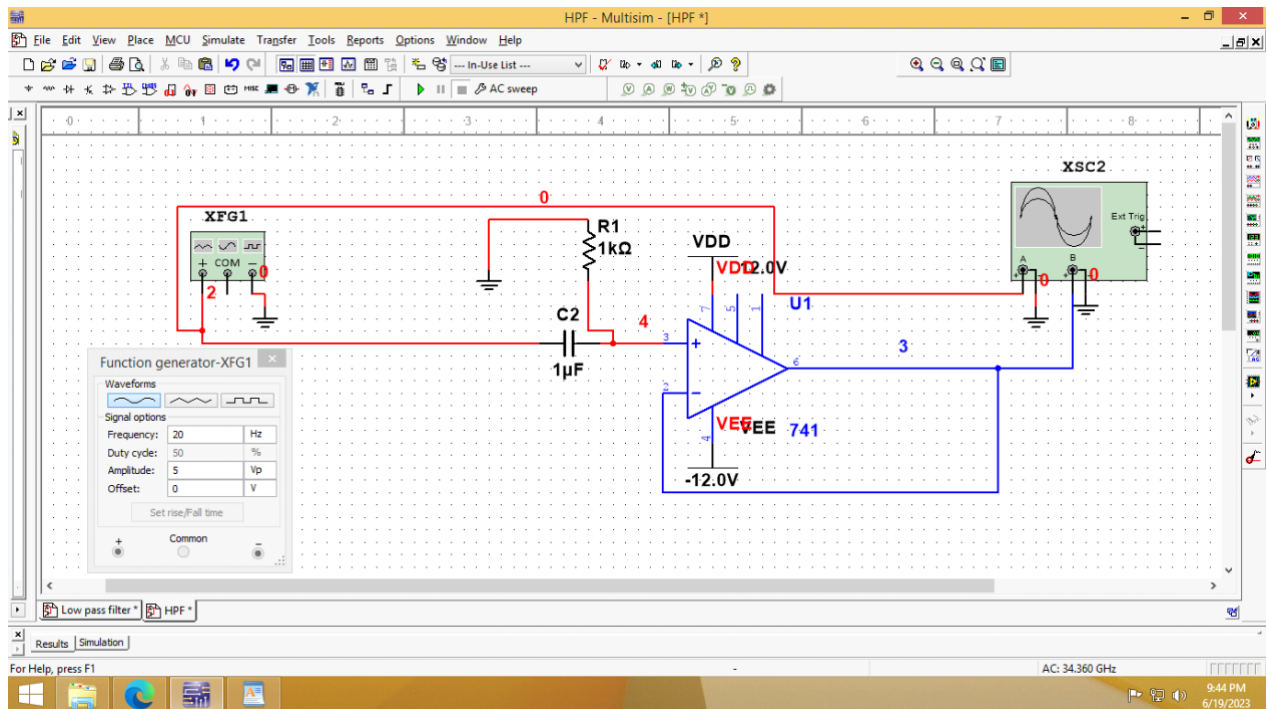
COMPONENTS: 1 Micro farad (1 capacitor), IC 741, 1K ohm(1 RESISTOR), CRO, FUNG GEN



Experiment: 5A) Second ORDER ACTIVE Low Pass Filter

AIM: Study and simulation of Second Order Low Pass filter and observing the output WAVEFORM using MULTISIM software worksheet



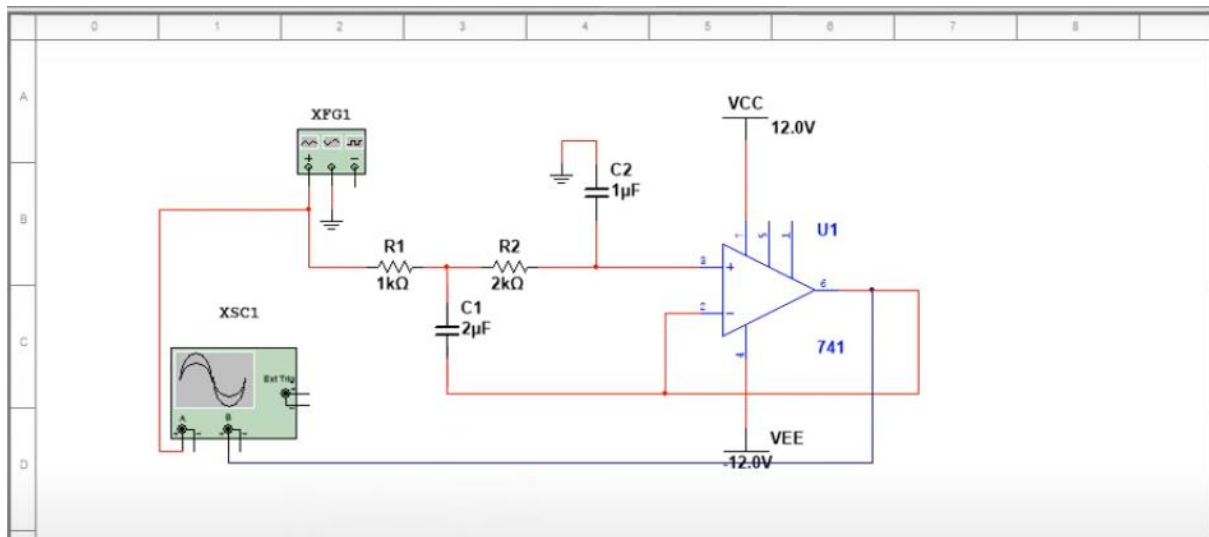
COMPONENTS: 1 Micro farad (1 capacitor), 2 Micro farad (1 capacitor), IC 741, 1K ohm(1 RESISTOR), 2K ohm(1 RESISTOR), CRO, FUNG GEN



$$f_c = \frac{1}{2\pi (\sqrt{R_1 C_1 R_2 C_2})}$$

$$= \frac{1}{2 \times 3,14 \times \sqrt{(1 \times 10^3) \times (2 \times 10^{-6}) \times (2 \times 10^3) \times (1 \times 10^{-6})}}$$

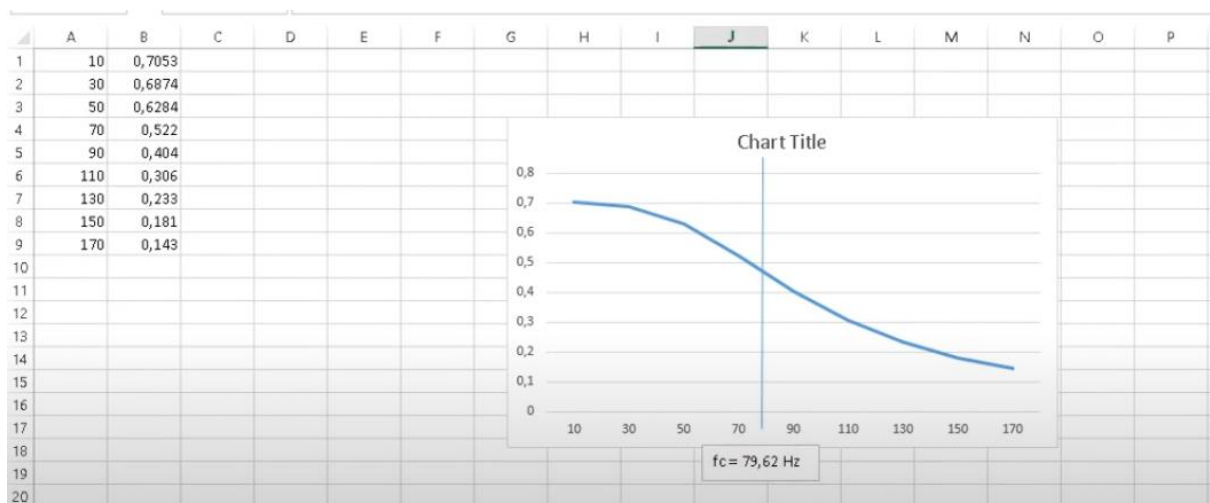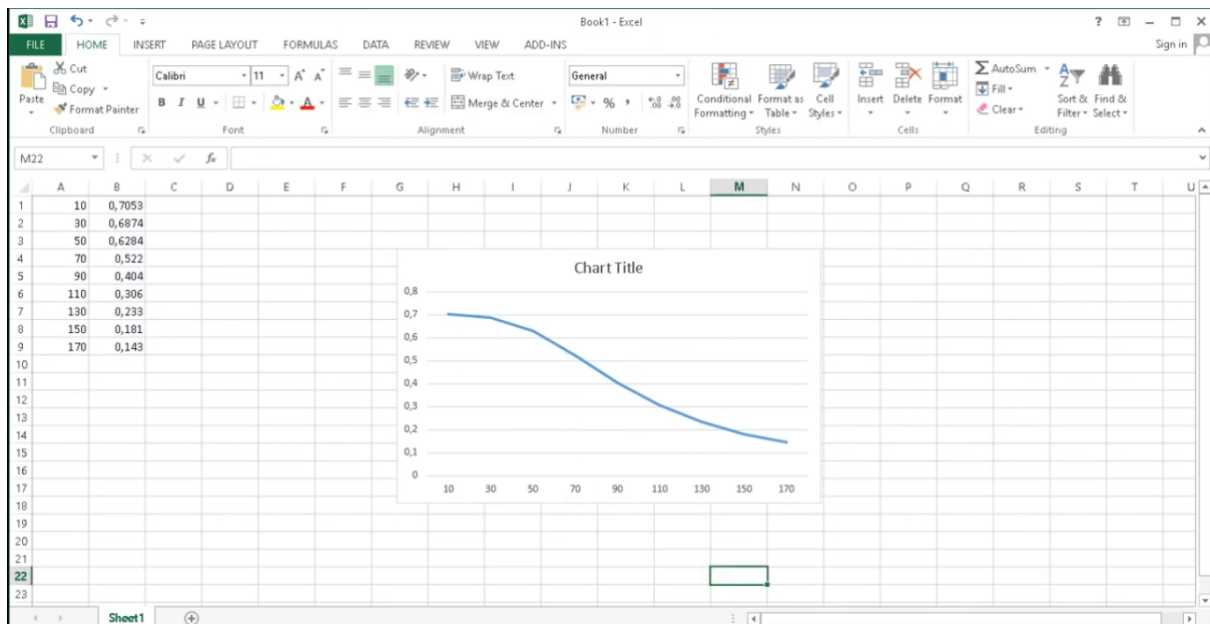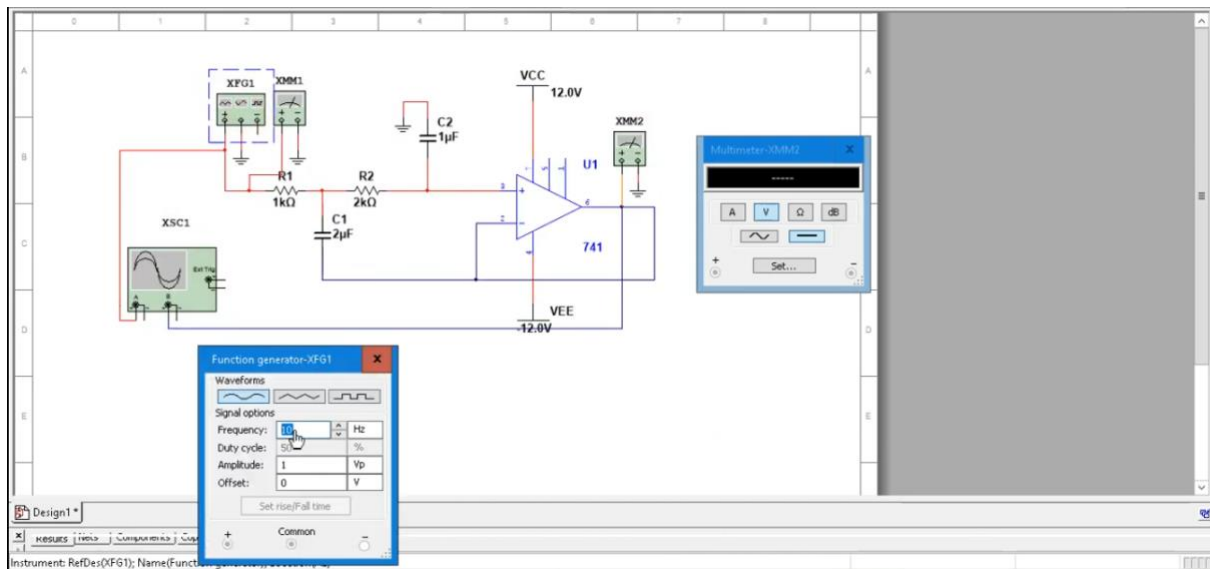
$$= \frac{1}{0,01256} = 79,62 \text{ Hz}$$





Experiment: 5B) Second ORDER ACTIVE High Pass Filter

AIM: Study and simulation of Second Order High Pass filter and observing the output WAVEFORM using MULTISIM software worksheet

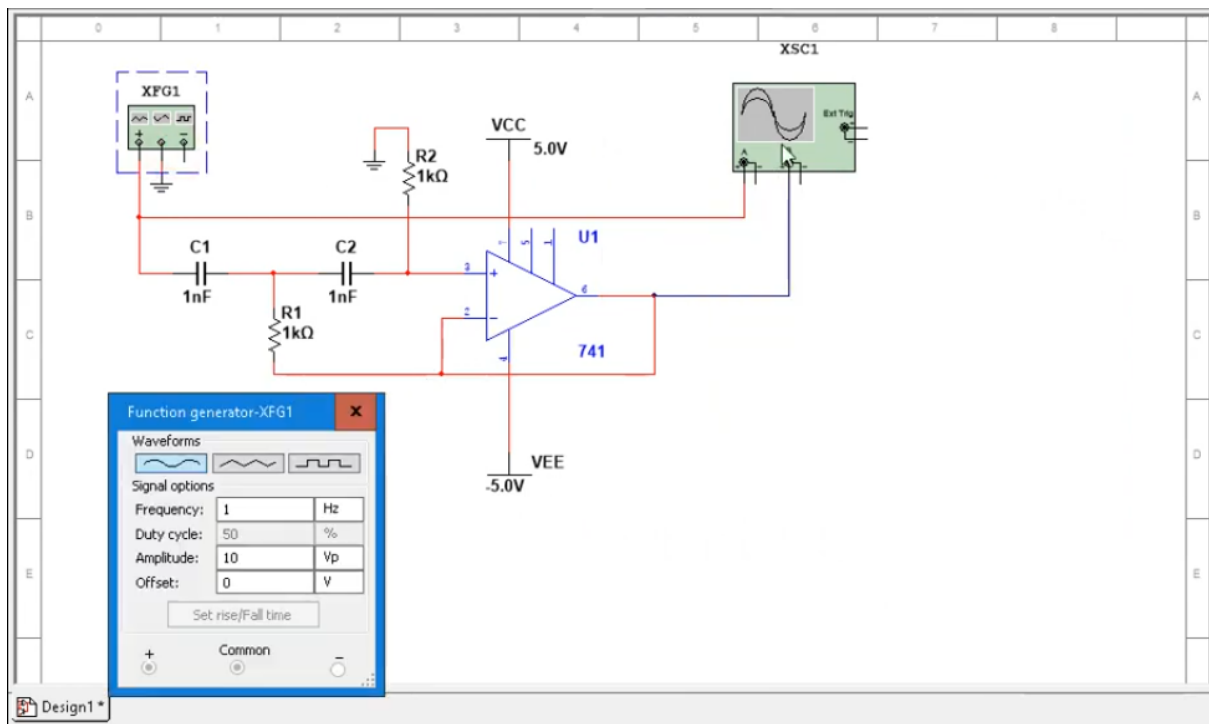COMPONENTS: 1 Nano farad (2 capacitor), IC 741, 1K ohm(2 RESISTOR), CRO, FUNG GEN



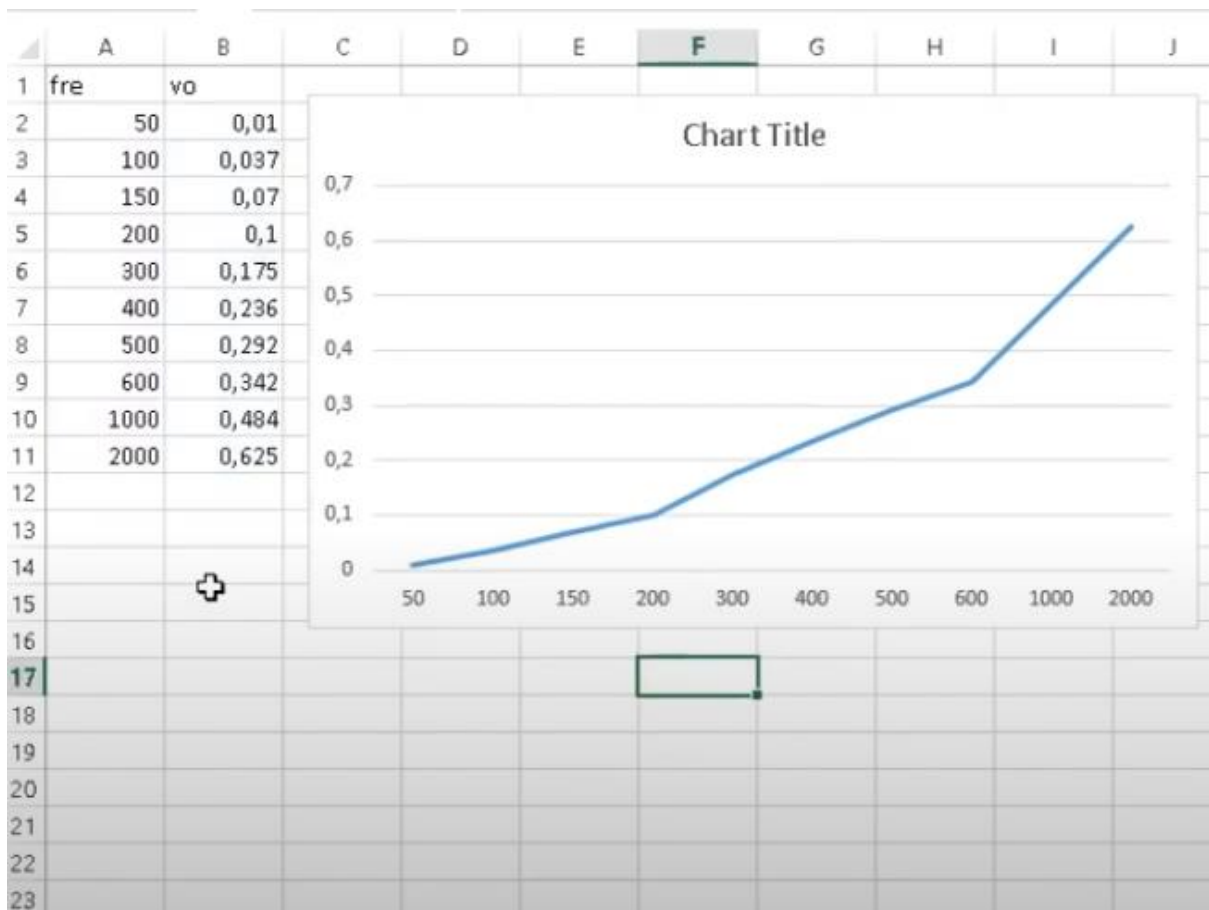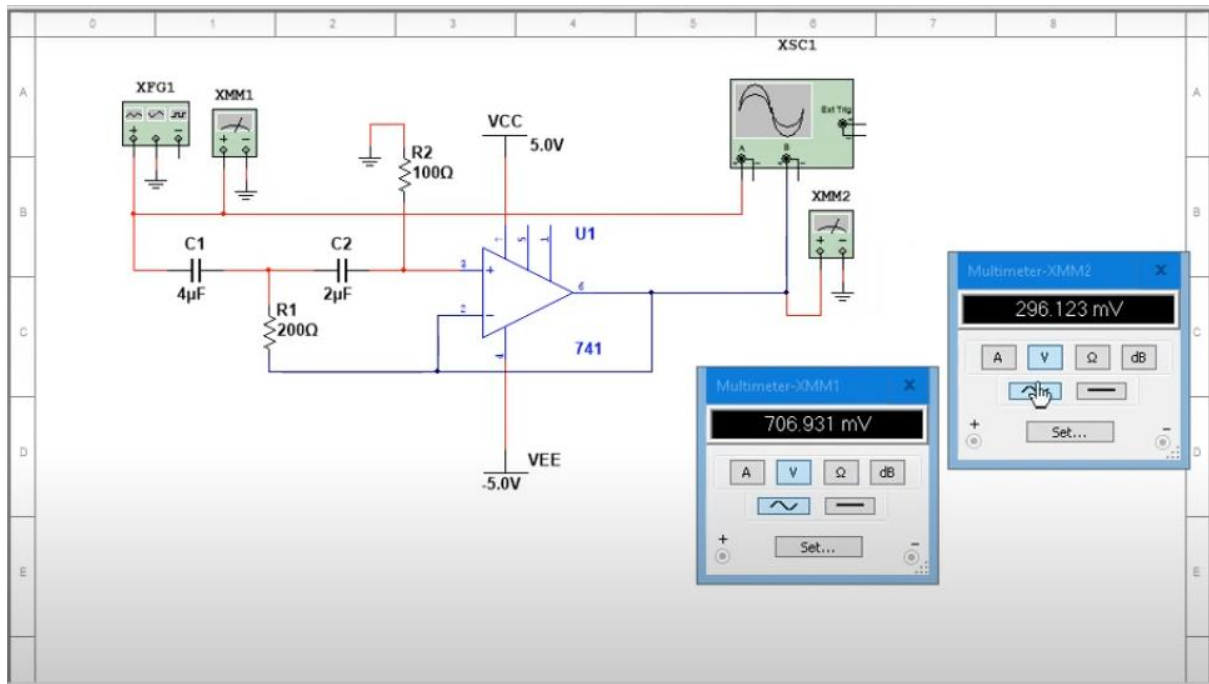
$$f_c = \frac{1}{2\pi\sqrt{R_1C_1R_2C_2}} = \frac{1}{2 \cdot 3,14 \cdot \sqrt{200 \cdot 4 \cdot 10^{-6} \cdot 100 \cdot 2 \cdot 10^{-6}}}$$
$$= \frac{1}{0,002512} = \underline{\underline{398,09 \text{ Hz}}}$$




Experiment: 6 Astable Multivibrator

AIM: To design the astable multivibrator using IC555 timer and to find out the ON and OFF time

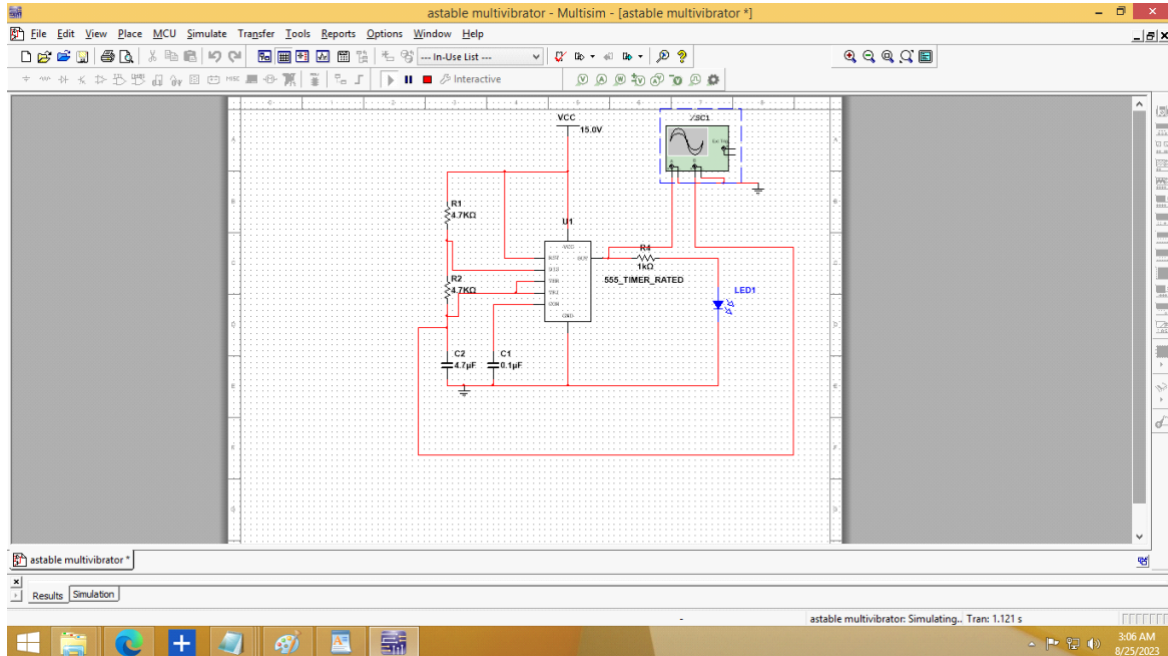COMPONENTS: 555 timer IC , resistor , capacitor ,Oscilloscope , LED.




Design:

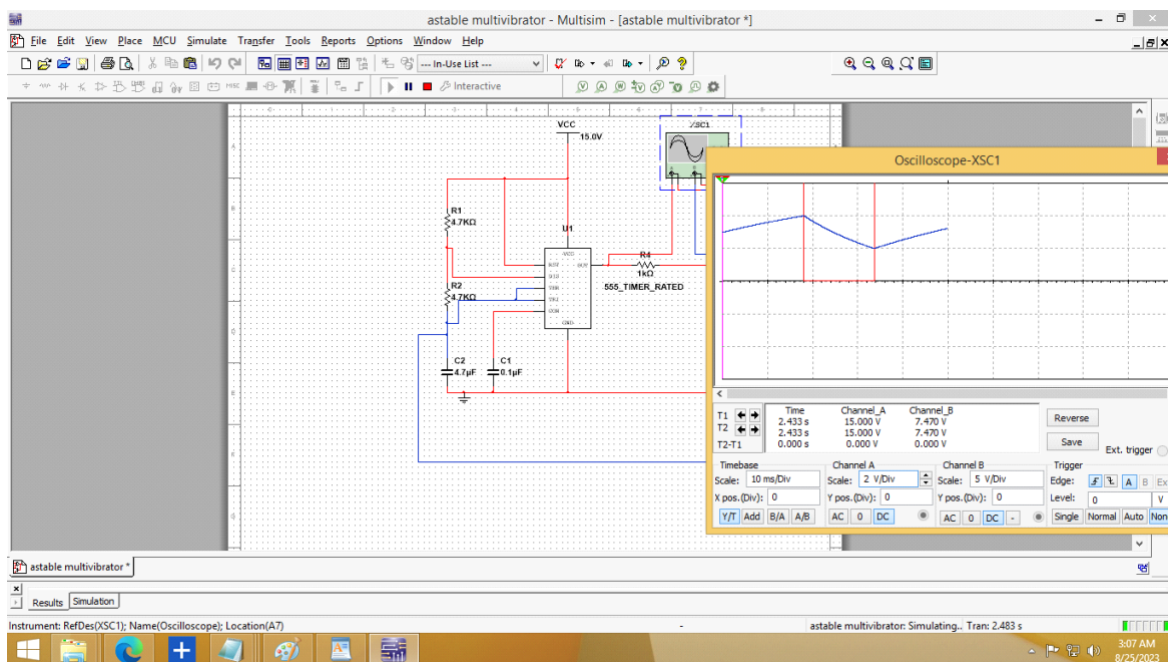

Experiment :7 Monostable Multivibrator

AIM: To design the monostable multivibrator using IC555 timer and to find out the ON and OFF time

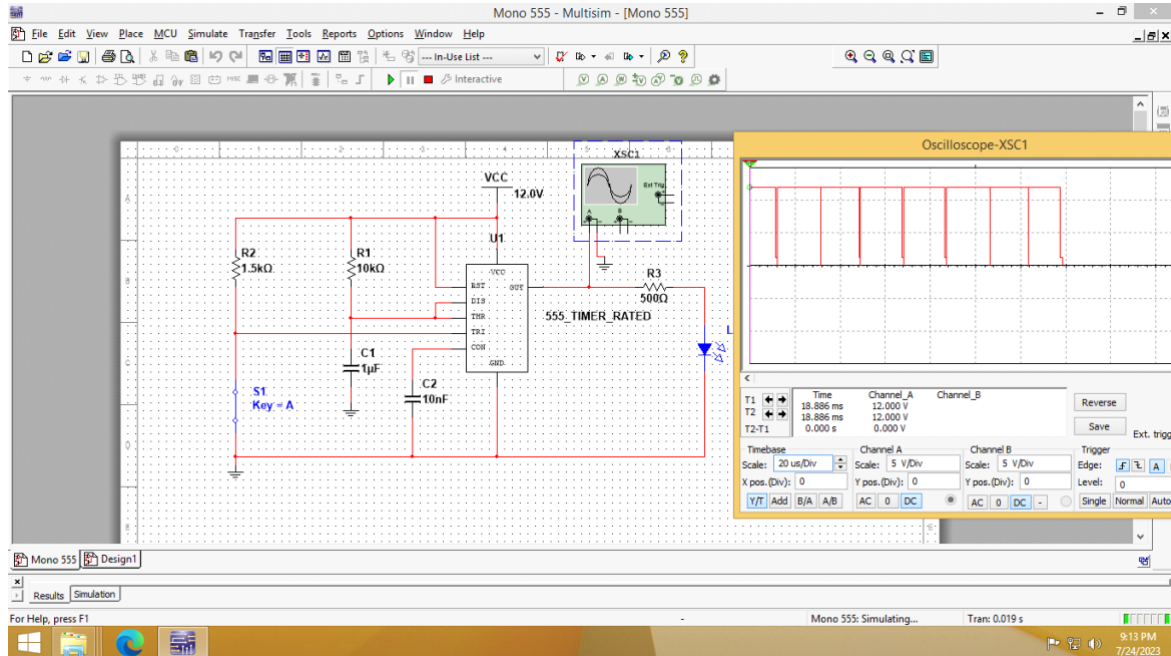COMPONENTS: 555 timer IC , resistor , capacitor ,Oscilloscope , LED.





Design: $T = 1.1R_1C_1$

Let $R_1 = 10k\Omega$; $C_1 = 1\mu F$ $T = 11ms$

Experiment :8) Inverting Schmitt Trigger

AIM: To design Inverting Schmitt Trigger using 741 and observing the output WAVEFORM using MULTISIM software worksheet

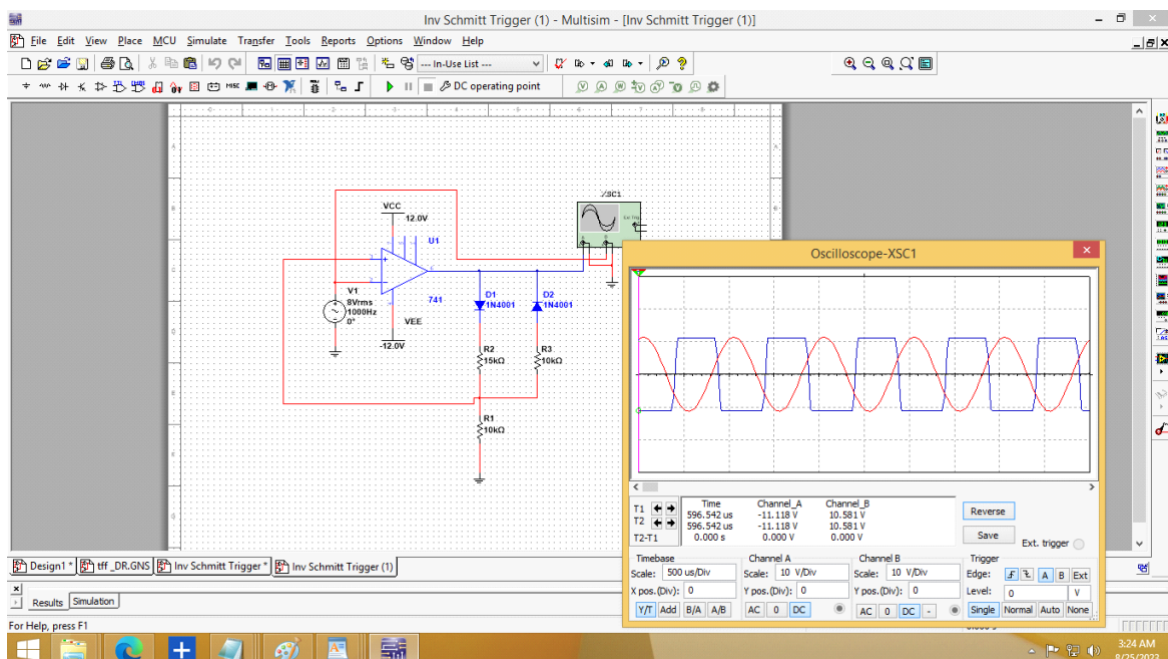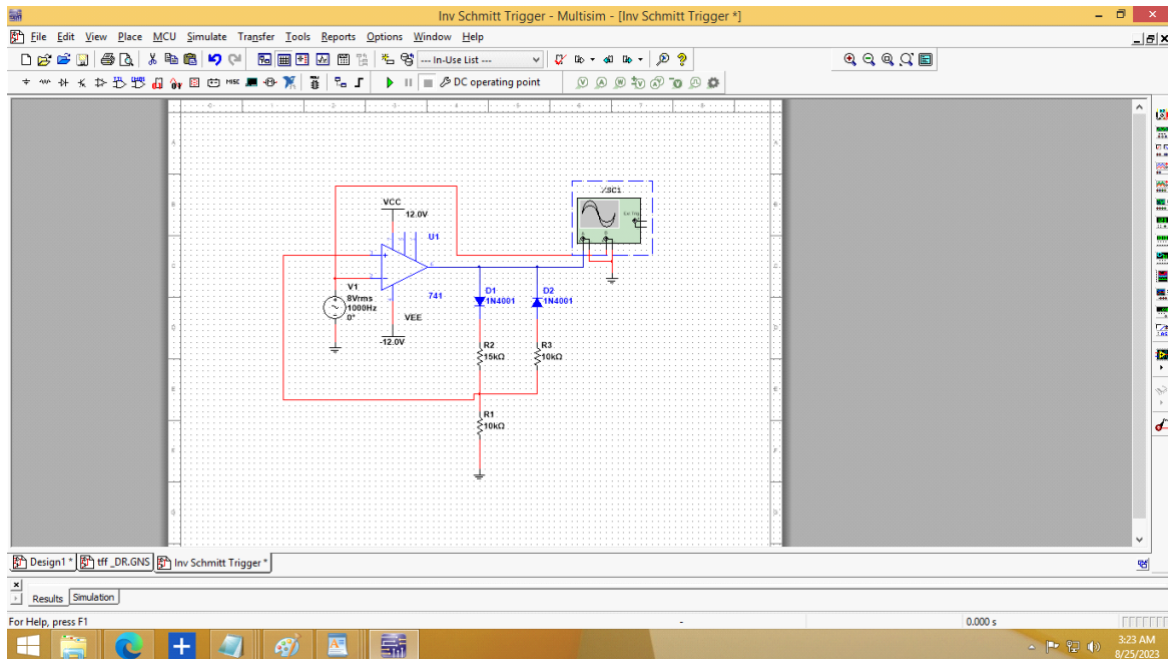COMPONENTS: 741 op-amp , resistor , capacitor ,Oscilloscope , LED.




Design given separately

Experiment :9) Non-Inverting Schmitt Trigger

AIM: To design Non Inverting Schmitt Trigger using 741 and observing the output WAVEFORM using MULTISIM software worksheet

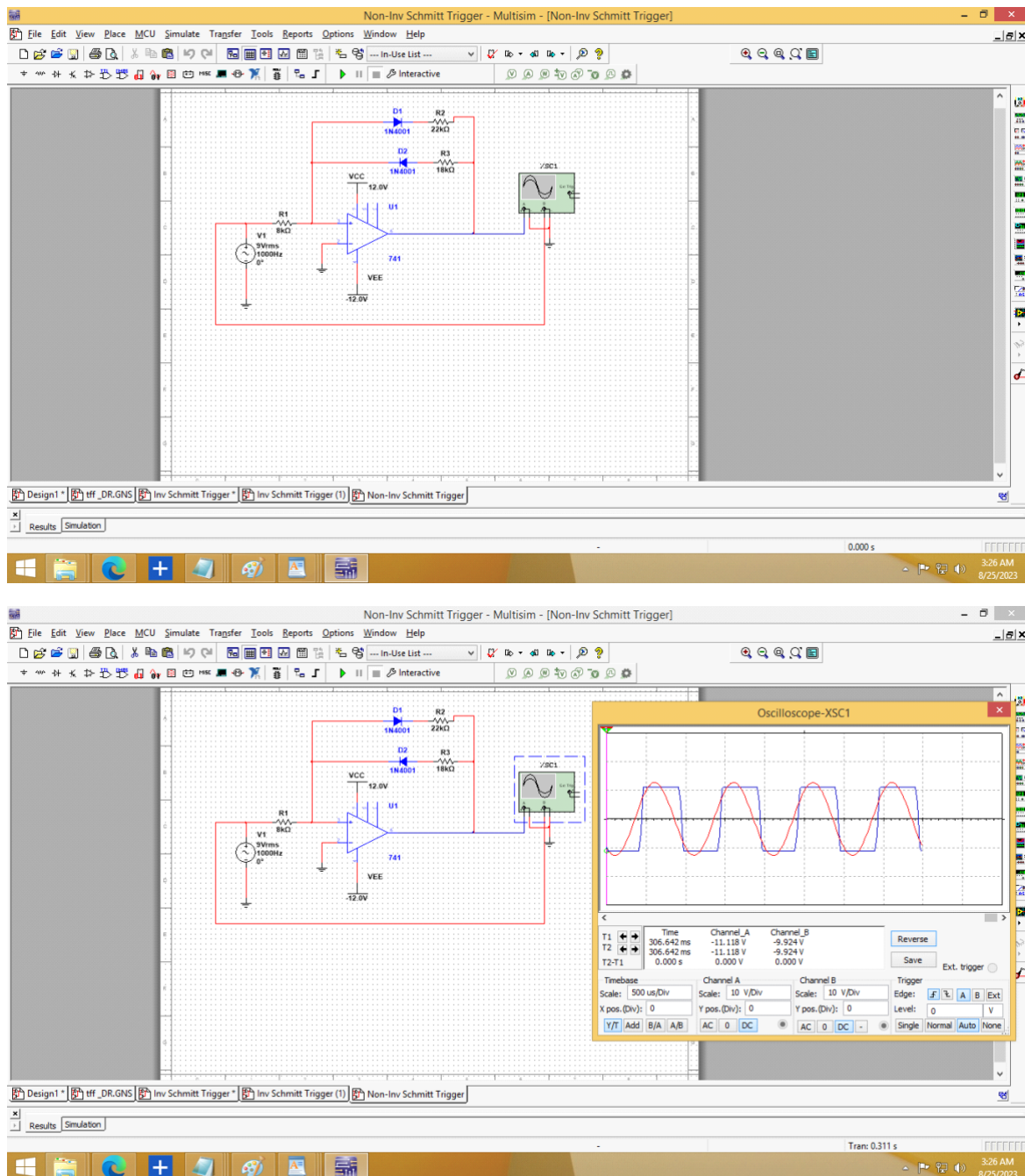COMPONENTS: 741 op-amp , resistor , capacitor ,Oscilloscope , LED.




Design given separately

Experiment :10) D-Flip Flop Realization

AIM: To design D-Flip Flop and verify the output with truth table

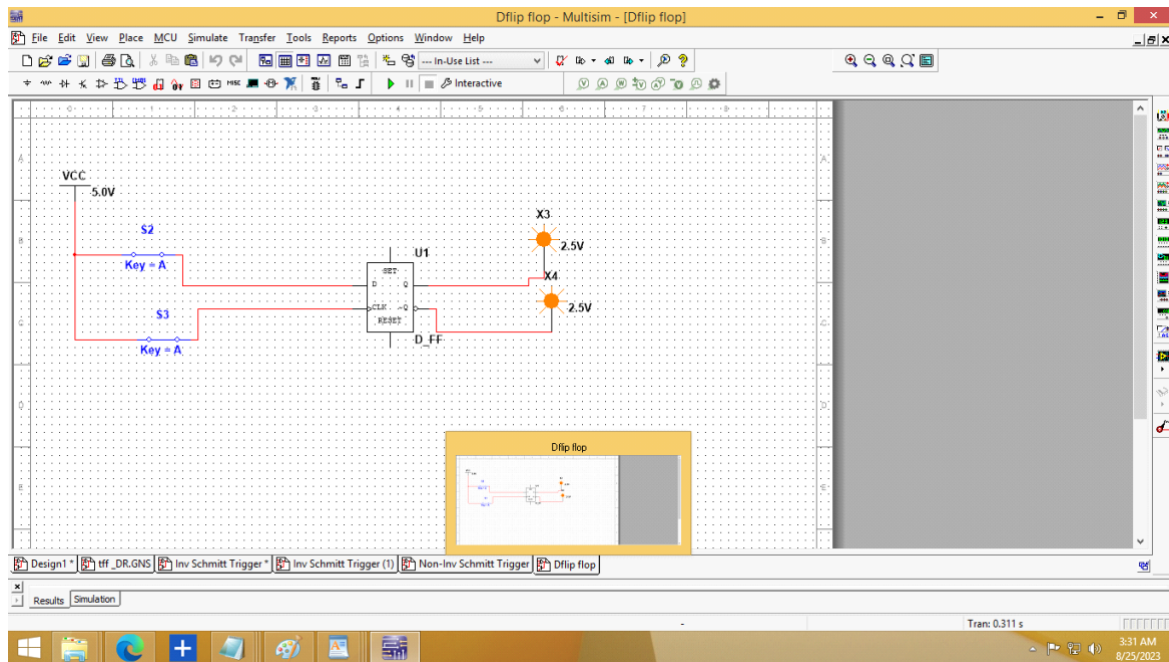
COMPONENTS: D-Flip Flop , Vcc, Switch ,Probe.



Experiment :11) T-Flip Flop Realization

AIM: To design T-Flip Flop and verify the output with Case.

COMPONENTS: T-Flip Flop , Digital clock ,Interactive Digital Constant.

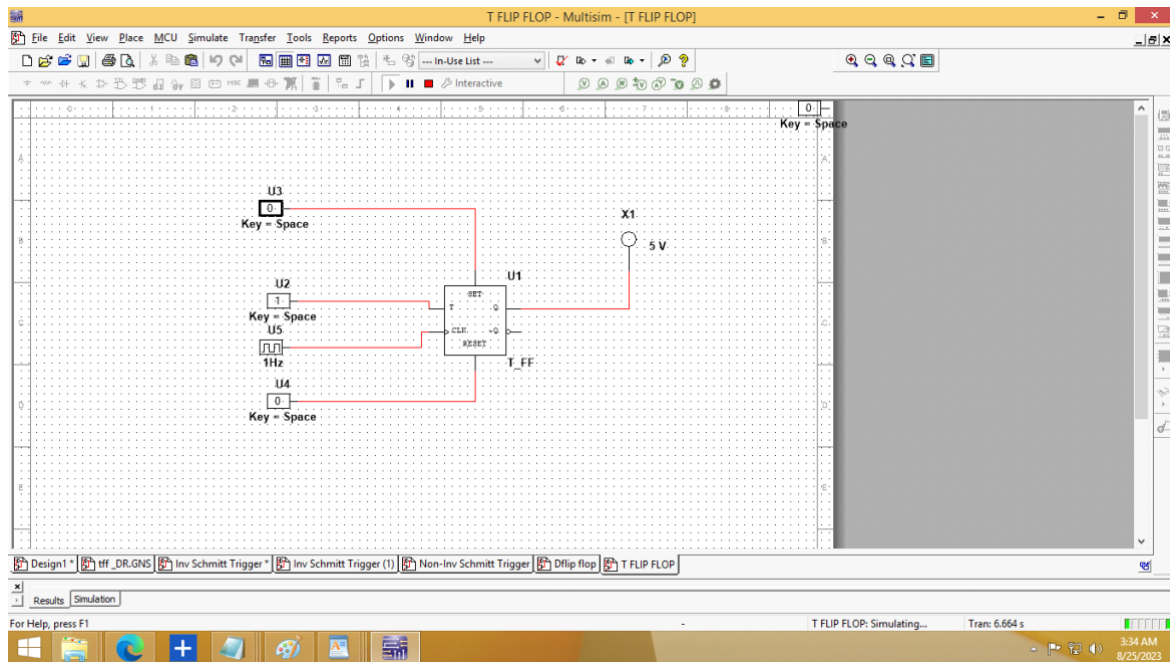


Experiment 12: Code Conversions

AIM: To design code converter and verify the output for binary to Gray code conversion.

COMPONENTS: Oscilloscope , Function Generator ,Op Amp 741.

Circuit Diagram

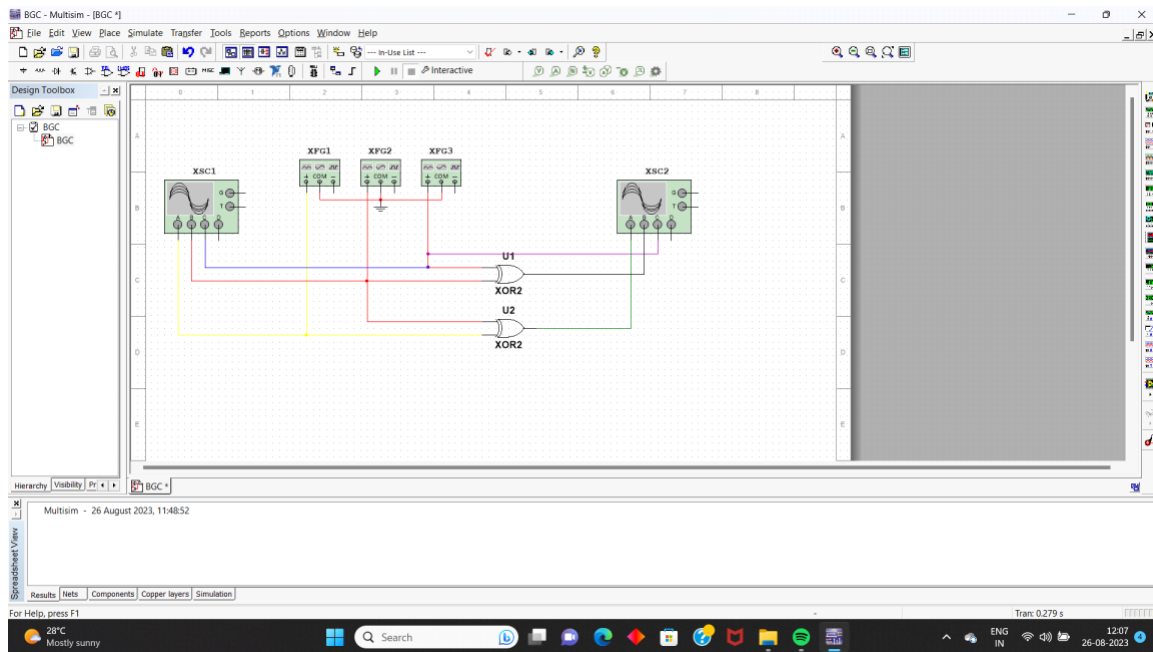

Waveforms

